

1 Instructions set:

Instruction	Opcode	Explanation
LDA	0001	It stores the data located in RAM into Accumulator register
LDB	0110	It stores the data located in RAM into register B
STR	0101	It stores output of arithmetic logic unit into RAM
ADD	0010	It adds the register A and register B and the added value is seen from ALU output.
SUB	0011	It subtracts register B from register A and the subtracted value is seen from ALU output.
AC_OUT	0100	It loads the value of register A into output register.
HLT	1111	It halts the program.

2 Control Sequencer:

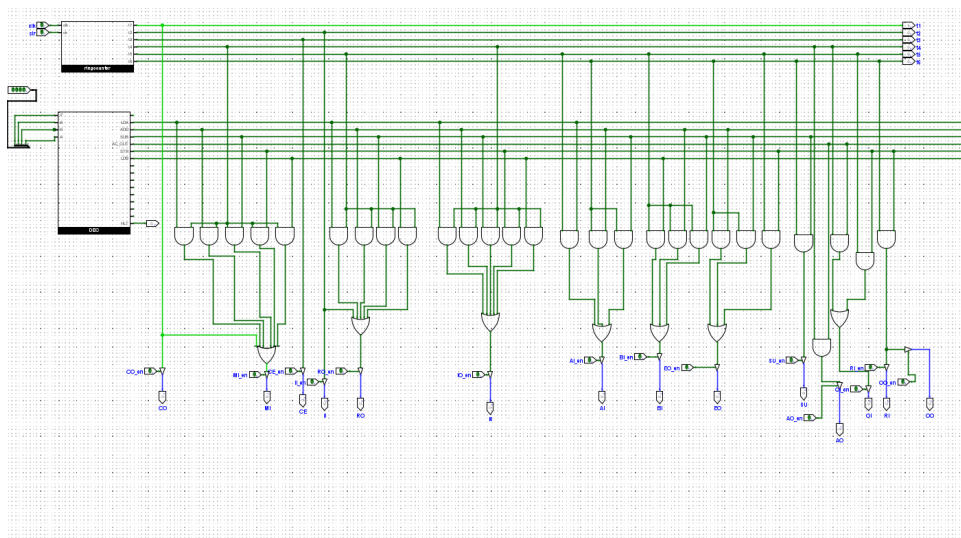


Figure 1: Final Layout of Control Sequencer

3 Pin Explanation:

Pin	Explanation
IO	Instruction register output enable
II	Instruction register input enable
AI	Register A input enable
BI	Register B input enable
AO	Register A output enable
OO	Output Register output enable
OI	Output Register input enable
EO	Alu output enable
SU	Subtraction enable
RI	Ram input(sram wr)
RO	Ram output(sram rd)
CO	Program counter output enable
CE	Program counter enable
MI	Mar in enable

4 Layout:

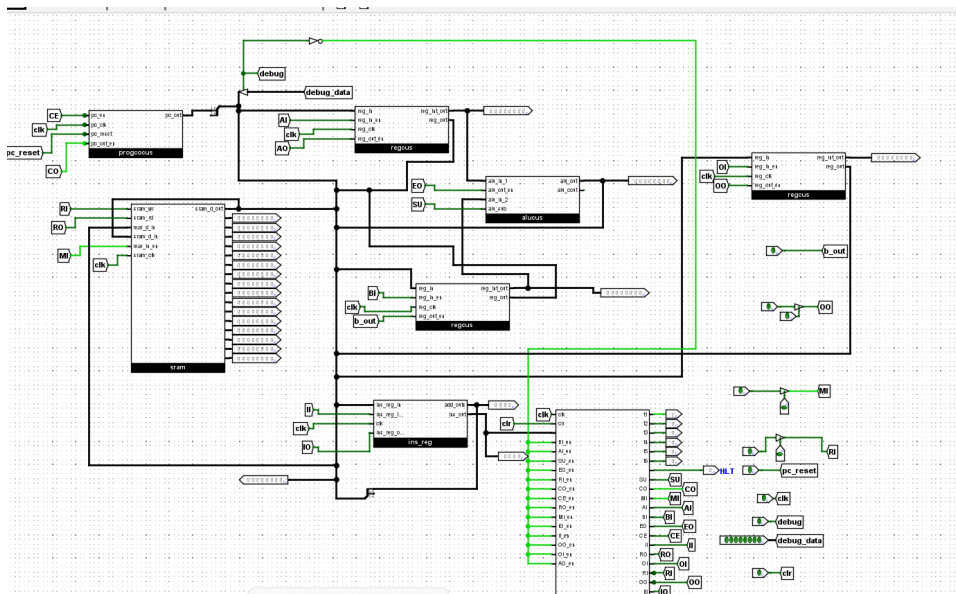


Figure 2: Final layout

Data Load:LDA 2(DATA 3)

- Turing on debug pin and resetting the program counter the program was started. When debug data was given 0000 0000 bus loaded with the data .When mar_in_en was turned on and clock pulse were given, the data loaded on the memory address register then turned off mar_in_en. RAM knew the work would be done on 0000 0000 address.

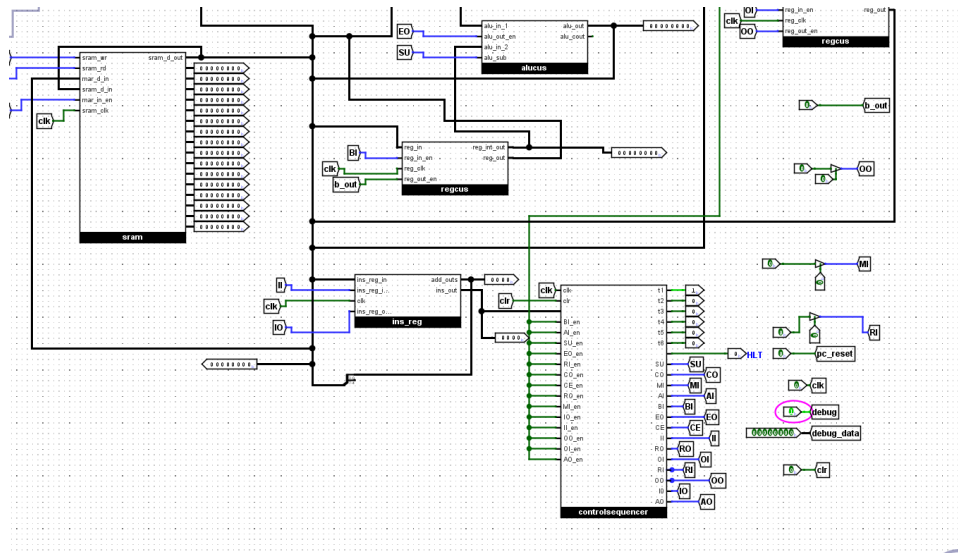


Figure 3: Debugging initialize

- Debug data was given 00010010(LDA 2) bus loaded with the data and sram_wr was turned on and clock pulse were given then the data 00010010 was saved on memory address 00000000 then sram_wr were turned off. That means at first which memory address would save the data were given then the saved data were given. Here 0001 was LDA and 0010 were memory address.

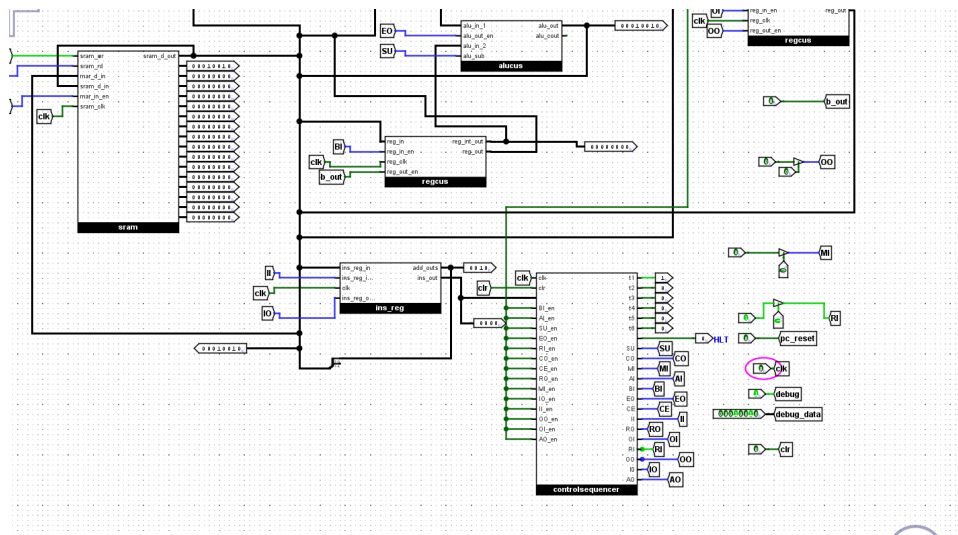


Figure 4: LDA 2 loaded

- When debug data was given 00000010 bus loaded with the data .When mar_in_en was turned on and clock pulse given, the data loaded on the memory address register then turned off mar_in_en. RAM knew the work would be done on 00000010 address.
- Debug data was given 00000011 bus loaded with the data and sram_wr was turned on and clock

pulse were given then the data 00001111 was saved on memory address 00000010 then sram_wr were turned off. Then debug pin were turned off.

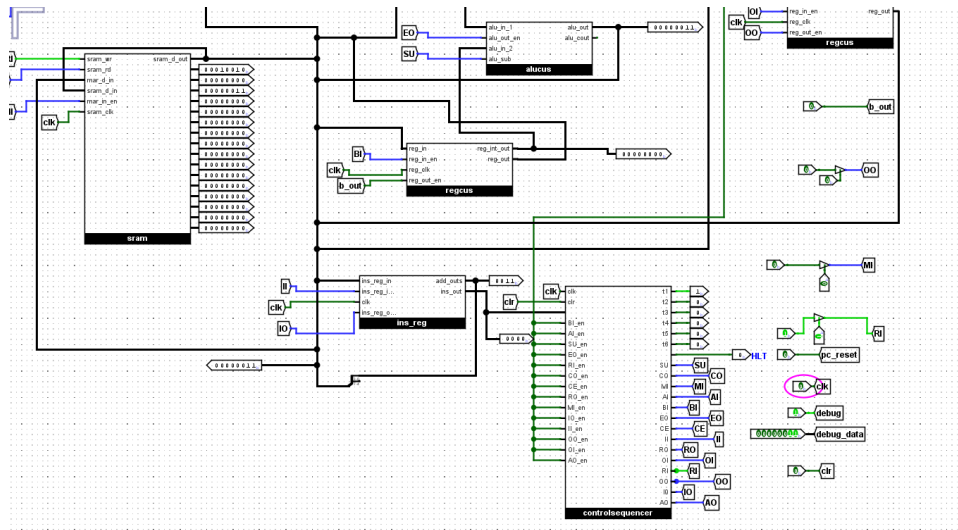


Figure 5: Data 3(00000011)loaded on address 2

Fetch:

- The program counter was reset to 0000. Clr pin were turned On.
- **T1:** Giving clock pulse, CO MI on
- **T2:** Giving clock pulse, RO II on
- **T3:** Giving clock pulse, CE on

Decode:

- This state was not sequential logic so no T states or clock pulse were required and here only combinational logic were executed.

Execute:

- **T4:** Giving clock pulse, IO MI on
- **T5:** Giving clock pulse, AI RO on. Accumulator register were loaded with 00000011.

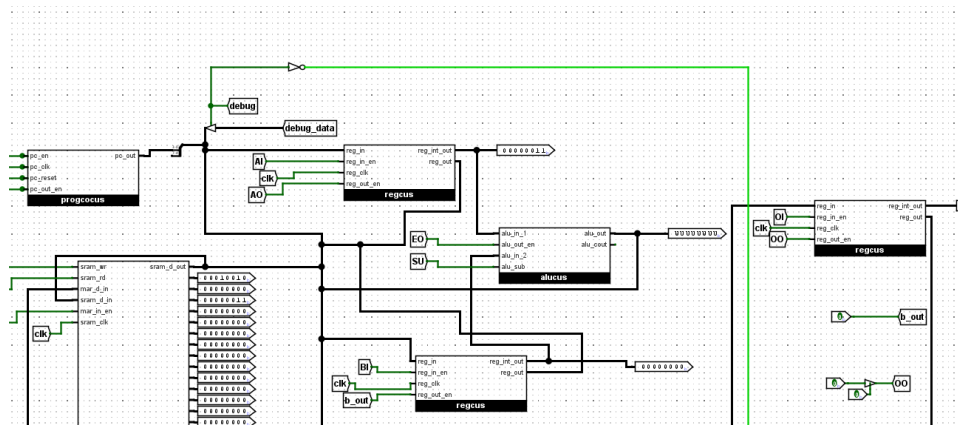


Figure 6: Accumulator Loaded with data

Data Load:LDB 1(DATA 2)

- Same as LDA 2 .Here the instruction 0110 0001(0110 is opcode of LDB and 0001 memory address) were given to load data 0000 0010 (saved on memory address 0000 0001)into register B. Here instead of AI ,BI were on at T5 state to save data on register B.At T6 state EO were ON so alu output were seen.

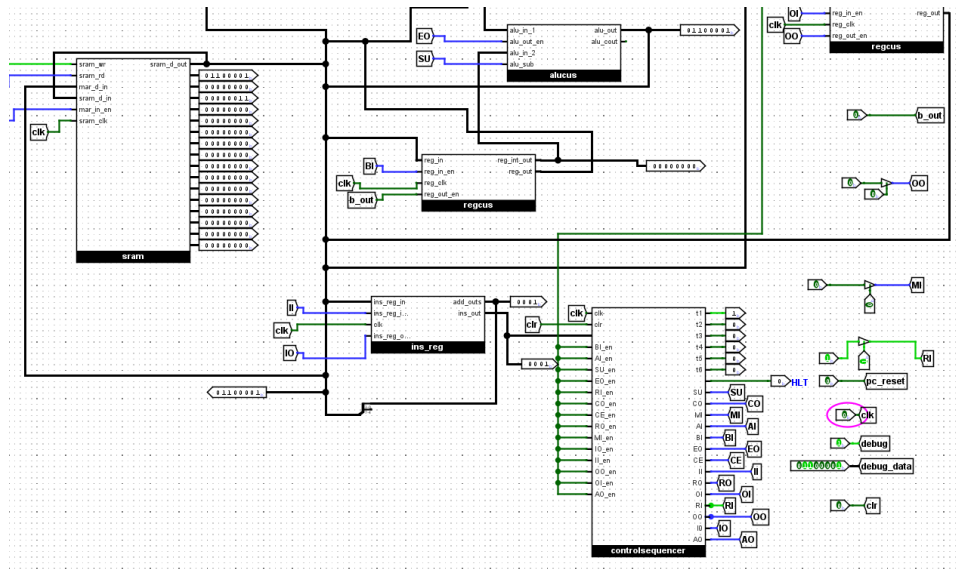


Figure 7: LDB 1 loaded

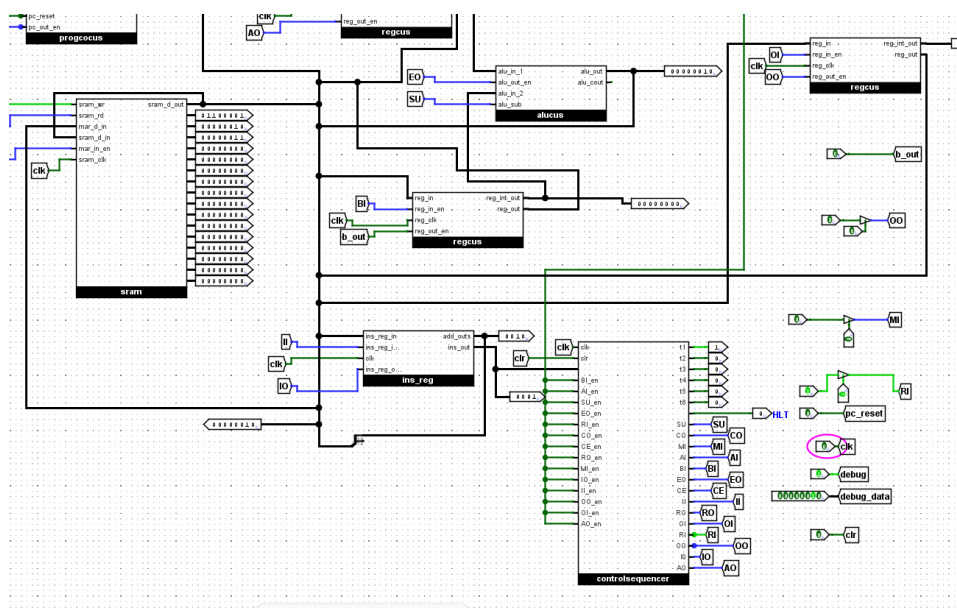


Figure 8: Data 2(00000010)loaded on address 1

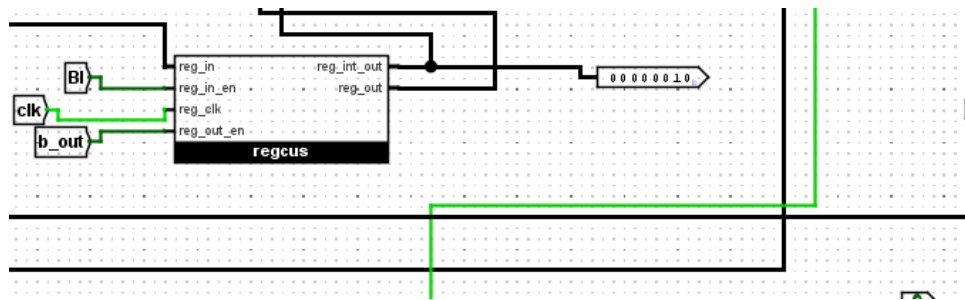


Figure 9: Register B Loaded with data

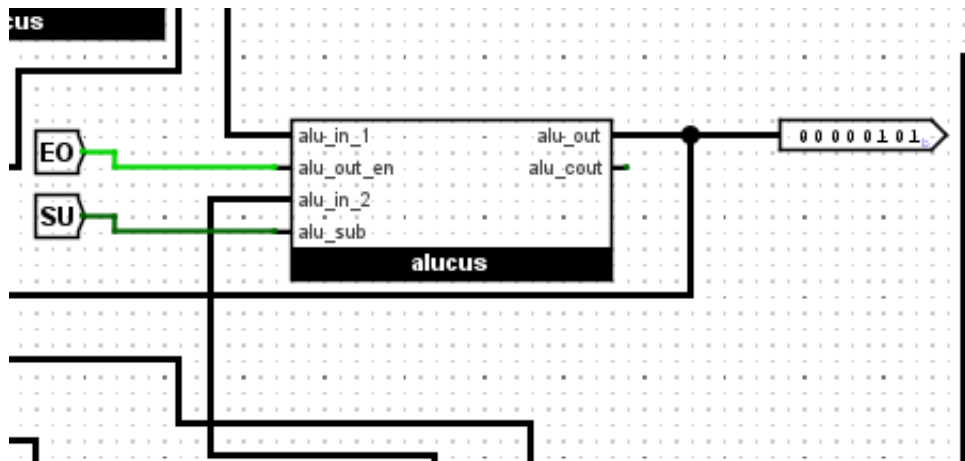


Figure 10: ALU output

ALU DATA STORE:

- Debug pin were turned on debug pin were set 0000 0000. When mar_in_en was turned on and clock pulse were given, the data loaded on the memory address register then turned off mar_in_en. RAM knew the work will be done on 0000 0000.
- Debug data was given 0101000 bus loaded with the data and sram_wr was turned on and clock pulse were given then the data 01010000 was saved on memory address 00000000 then sram_wr were turned off. Here 0101 was opcode of STR.

Fetch:

- The program counter was reset to 0000. Clr pin were turned On.
- **T1:** Giving clock pulse, CO MI on
- **T2:** Giving clock pulse, RO II on
- **T3:** Giving clock pulse, CE on

Decode:

- This state was not sequential logic so no T states or clock pulse were required and here only combinational logic were executed.

Execute:

- **T4:** Giving clock pulse, IO MI on
- **T5:** Giving clock pulse, EO OI on. Alu output were loaded on output register

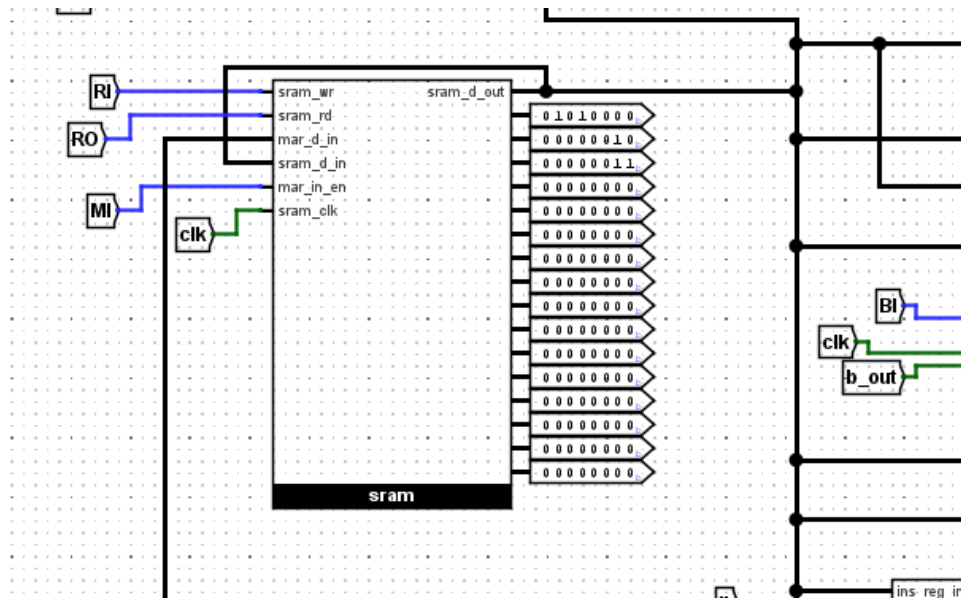


Figure 11: STR opcode loaded on 0 adress

- **T6:** Giving clock pulse, OO RI on so output register output enabled and data loaded on memory on 0000 0000 location

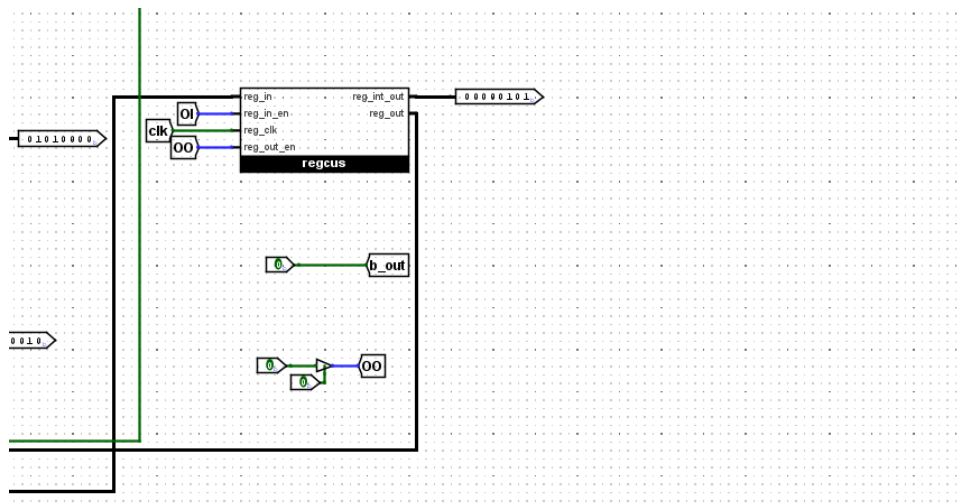


Figure 12: Output Register Loaded with ALU output

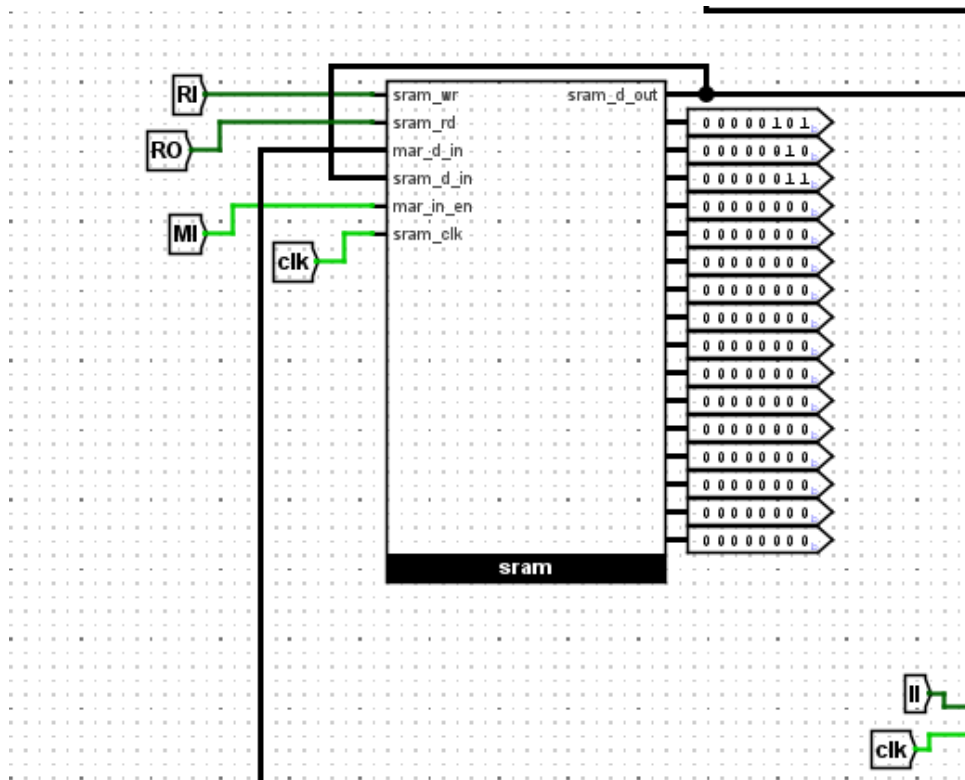


Figure 13: Alu output stored on Ram on address 0

ADD:

- Debug pin were truned on debug pin were set 0000 0000. When mar_in_en was turned on and clock pulse were given, the data loaded on the memory address register then turned off mar_in_en.RAM knew the work will be done on 0000 0000.
- Debug data was given 00100100 bus loaded with the data and sram_wr was turned on and clock pulse were given then the data 00100100 was saved on memory address 00000000 then sram_wr were turned off.Here 0101 was opcode of ADD.

 


Figure 14: ADD opcode loaded on 0 adress

- Debug pin were truned on debug pin were set 0000 0100. When mar_in_en was turned on and clock pulse were given, the data loaded on the memory address register then turned off mar_in_en.RAM knew the work will be done on 0000 0100.
- Debug data was given 00000100 bus loaded with the data and sram_wr was turned on and clock pulse were given then the data 00000100 was saved on memory address 00000100 then sram_wr were turned off.

Figure 15: Data loaded on adress 4

- The program counter was reset to 0000. Clr pin were turned On.
- **T1:**Giving clock pulse,CO MI on
- **T2:**Giving clock pulse,RO II on
- **T3:**Giving clock pulse,CE on

Decode:

- This state was not sequential logic so no T states or clock pulse were required and here only combinational logic were executed.

Execute:

- **T4:** Giving clock pulse, IO MI on
- **T5:** Giving clock pulse, RO BI on. Data loaded on register B.
- **T6:** Giving clock pulse, EO AI on so ALU output saved on register A.

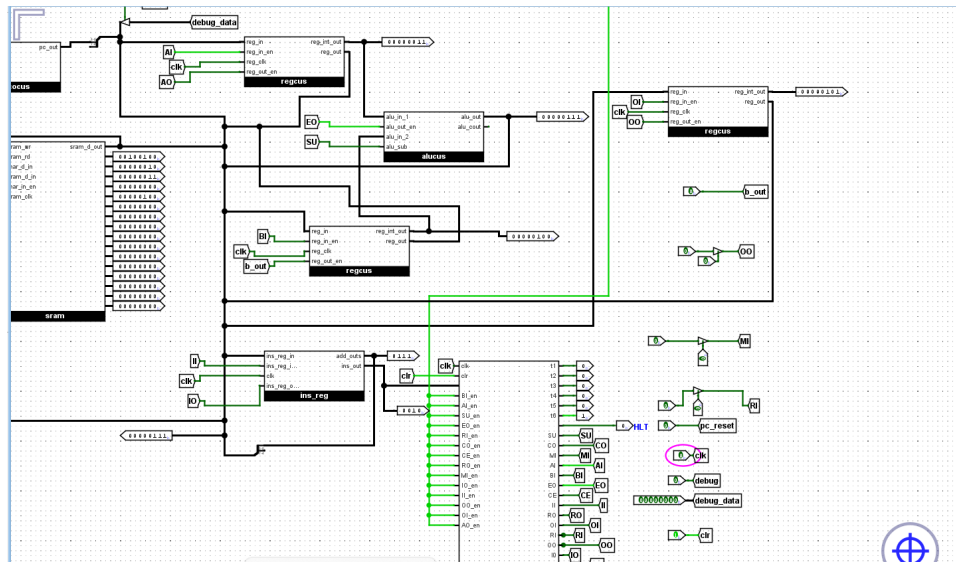


Figure 16: ALU output

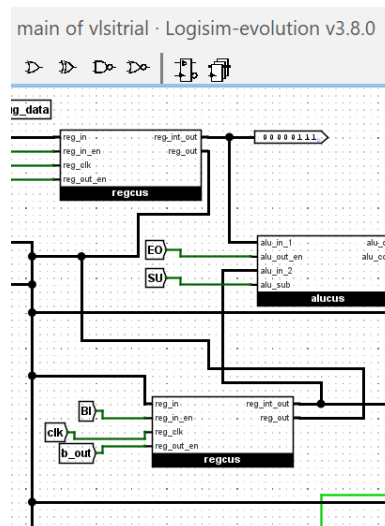


Figure 17: Register A loaded with Alu output